
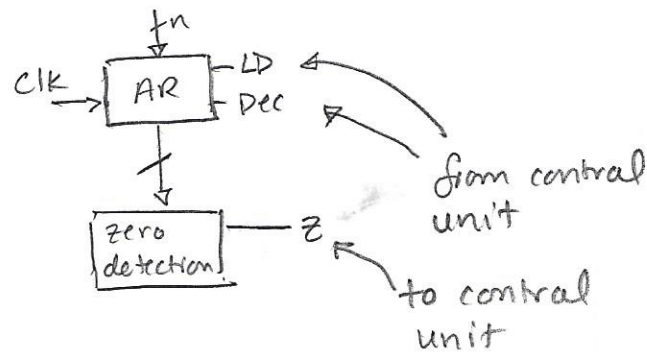


state A is the initial state  
 state B is the state where;  
 $BR \leftarrow \text{input A}$   
 $AR \leftarrow \text{input B}$   
 $PR \leftarrow 0$

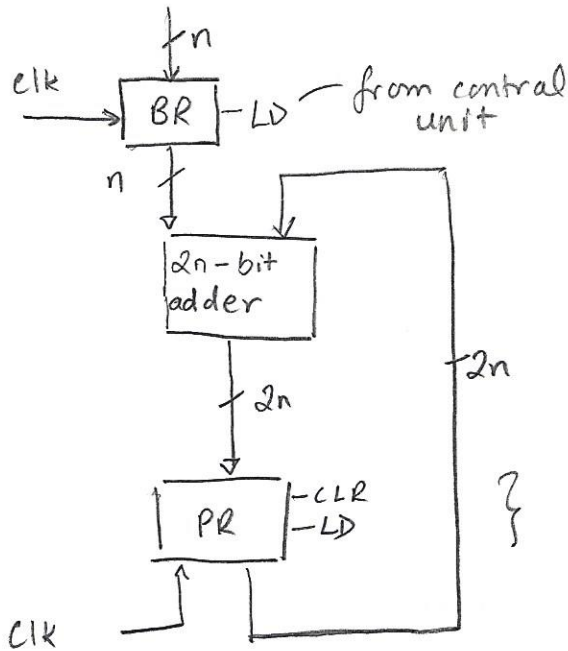
state C is the state where,  
 $PR \leftarrow BR + PR$   
 $AR \leftarrow AR - 1$




} CLR and LD are from the central unit

the internal architecture of the datapath consists of:

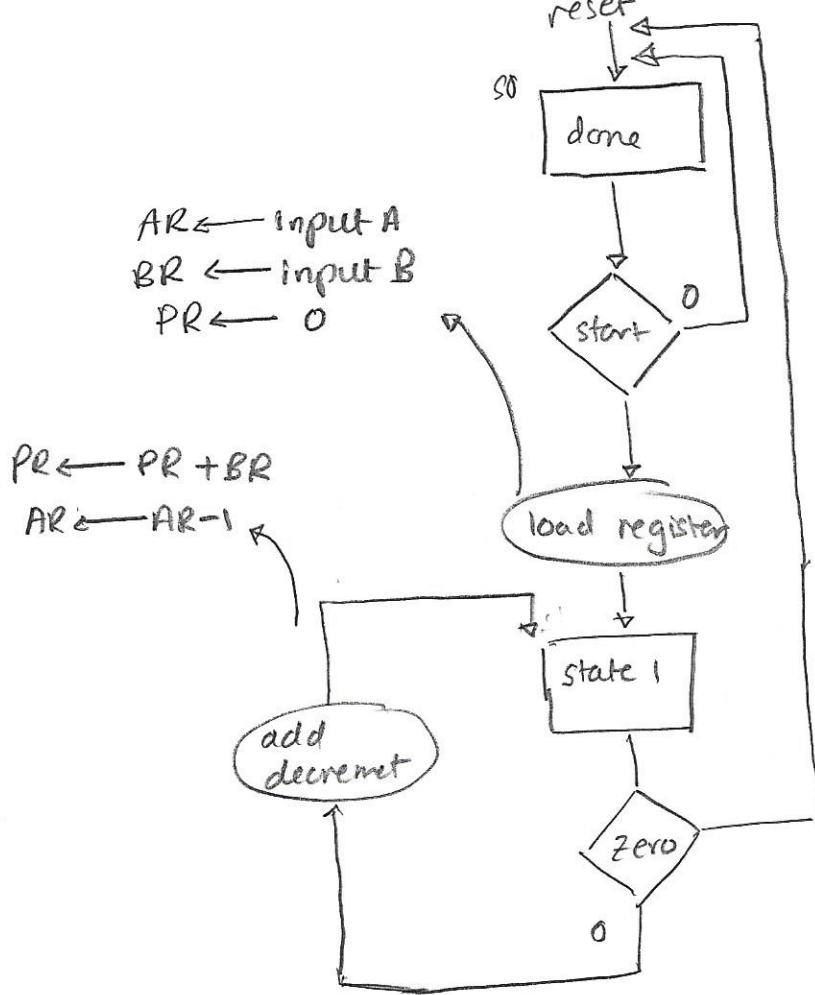- a double width register to hold product  $\rightarrow PR$
- a register to hold the multiplicand  $\rightarrow BR$
- double-width parallel adder
- single-width parallel adder for decrementing the multiplier unit




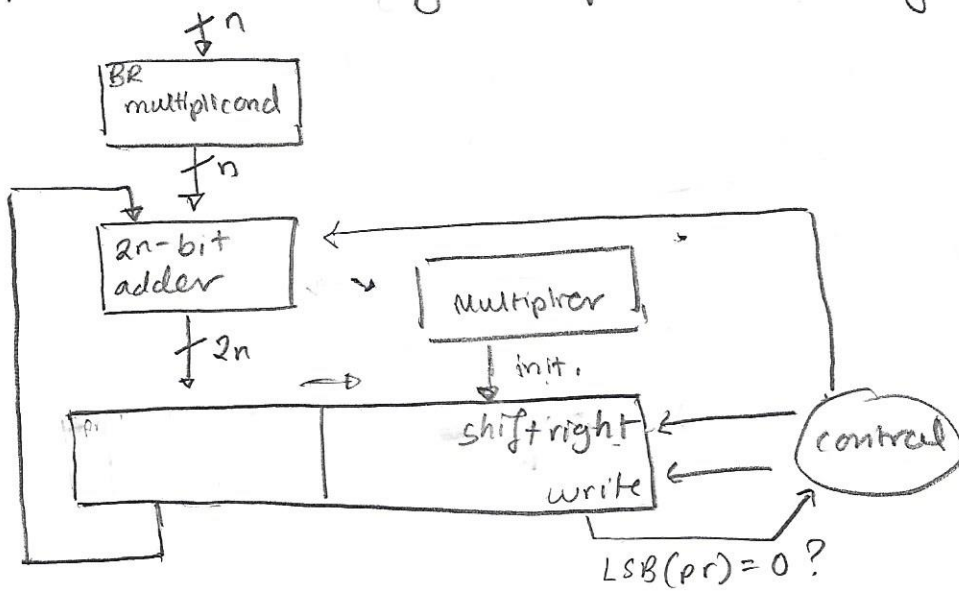This is the expected ASM and state diagram for the multiplier. The components for our approach is as follows:



Multiplicand register, adder, and multiplier register are all 4 bits wide, with only the product register left a 8-bits. Multiplier is placed in the right half of the product register.

Our approach :

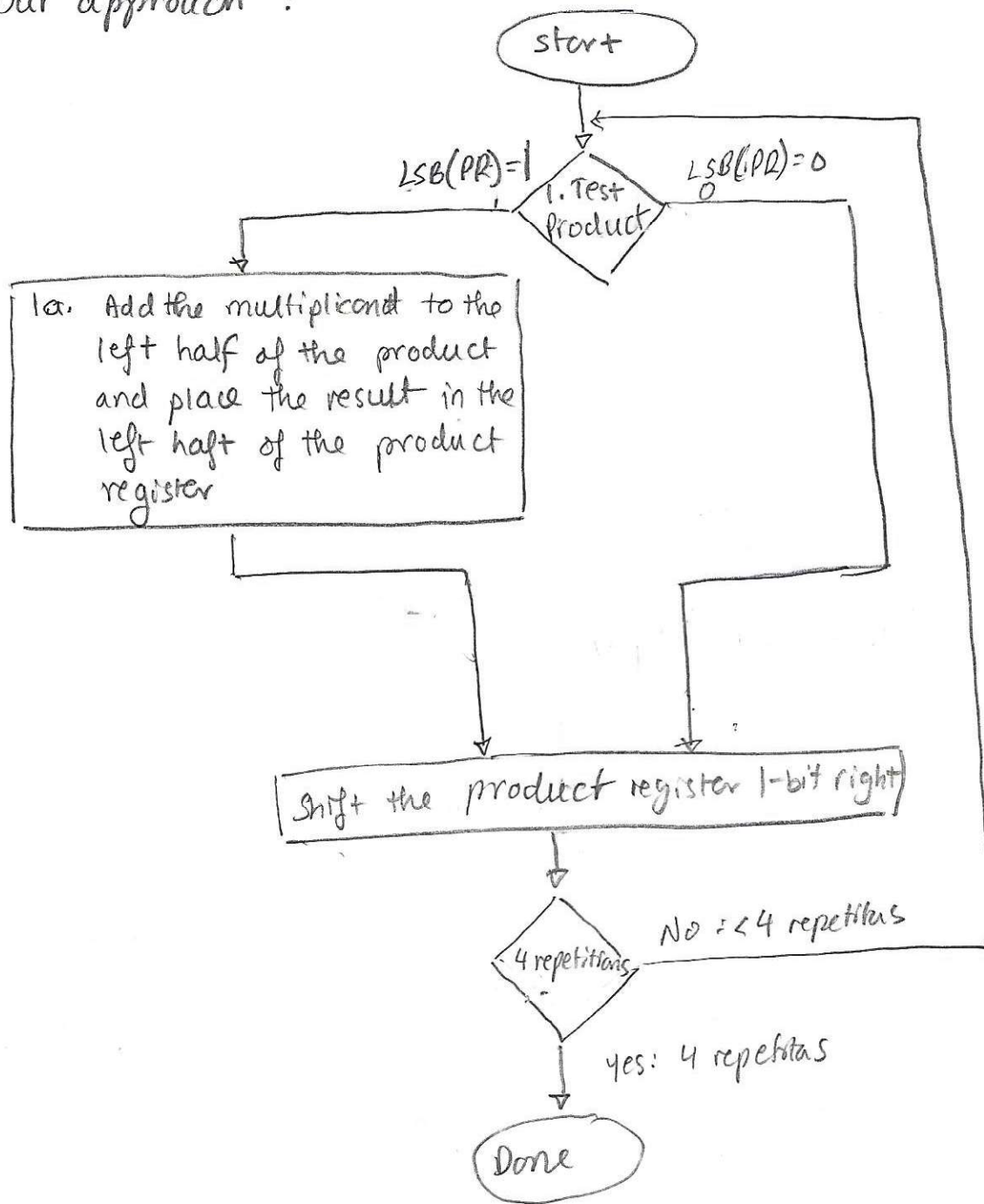

| Iteration | Step  | Multiplicand | Product                |
|-----------|---|--------------|------------------------|
| 0         | Initial values  | 0010         | 0000 0011              |
| 1         | 1: $a: 1 \Rightarrow \text{product} = \text{product} + \text{multiplicand}$<br>2: Shift right product | 0010<br>0010 | 0010 0011<br>0001 0001 |
| 2         | 1: $a: 1 \Rightarrow \text{product} = \text{product} + \text{multiplicand}$<br>2: Shift right product | 0010<br>0010 | 0001 1000<br>0000 1100 |
| 3         | 1: $0 \Rightarrow$ no operation<br>2: Shift right product   | 0010<br>0010 | 0000 1100<br>0000 0110 |
| 4         | 1: $0 \Rightarrow$ no operation<br>2: Shift right product   | 0010<br>0010 | 0000 1100<br>0000 0110 |

check:

$$\begin{array}{r}
 0011 \\
 \times 0010 \\
 \hline
 00000110 \\
 2^2 + 2^1 = 6
 \end{array}$$

$$\begin{array}{r}
 3 \\
 \times 2 \\
 \hline
 6
 \end{array}$$

| Iteration | Step  | Multiplicand | Product                |
|-----------|---|--------------|------------------------|
| 0         | Initial values  | 0010         | 0000 0011              |
| 1         | 1: $a: 1 \Rightarrow \text{product} = \text{product} + \text{multiplicand}$<br>2: Shift right product | 0010<br>0010 | 0010 0011<br>0001 0001 |
| 2         | 1: $a: 1 \Rightarrow \text{product} = \text{product} + \text{multiplicand}$<br>2: Shift right product | 0010<br>0010 | 0011 0001<br>0001 1000 |
| 3         | 1: $0 \Rightarrow$ no operation<br>2: Shift right product   | 0010<br>0010 | 0001 1000<br>0000 1100 |
| 4         | 1: $0 \Rightarrow$ no operation<br>2: Shift right product   | 0010<br>0010 | 0000 1100<br>0000 0110 |

check:

$$\begin{array}{r}
 0011 \\
 \times 0010 \\
 \hline
 00000110 \\
 2^2 + 2^1 = 6
 \end{array}$$

$$\begin{array}{r}
 3 \\
 \times 2 \\
 \hline
 6
 \end{array}$$